

Rajshahi University of Engineering & Technology

Course No: CSE 2204

Course Title: Sessional based on CSE 2203

Submitted To:

Md. Zahirul Islam Lecturer Department of Computer Science and Engineering Rajshahi University of Engineering and Technology	Prof. Dr. Boshir Ahmed Professor Department of Computer Science and Engineering Rajshahi University of Engineering and Technology
--	--

Submitted By:

Name: Mondol Mridul Provakar

Roll: 1803062

Section: B

Department of Computer Science and Engineering,
Rajshahi University of Engineering and Technology.

Date of Submission: 21 – 03 – 2021

Experiment No.: 4.1

4.1.1: Name of the experiment:

Implement Various Logic Functions (For Example

$F(a, b, c, d) = \text{SOP}(0, 2, 3, 4, 6, 10, 14, 15)$).

4.1.2: Objectives:

- To understand how to use the logisim software, test logic design and debug it.
- To study & implement various logic functions
- Simplifying logic circuit functions
- Understand how to implement simple circuits based on a schematic diagram using logic gates.

4.1.3: Theory:

A Boolean function is an algebraic form of Boolean expression. A Boolean function of n -variables is represented by $f(x_1, x_2, x_3, \dots, x_n)$. By using Boolean laws and theorems, we can simplify the Boolean functions of digital circuits. A brief note of different ways of representing a Boolean function is shown below.

- Sum-of-Products (SOP) Form
- Product-of-sums (POS) form
- Canonical forms

The sum-of-products (SOP) form is a method (or form) of simplifying the Boolean expressions of logic gates. In this SOP form of Boolean function representation, the variables are operated by AND (product) to

form a product term and all these product terms are ORed (summed or added) together to get the final function.

A sum-of-products form can be formed by adding (or summing) two or more product terms using a Boolean addition operation. Here the product terms are defined by using the AND operation and the sum term is defined by using OR operation.

The sum-of-products form is also called as Disjunctive Normal Form as the product terms are ORed together and Disjunction operation is logical OR. Sum-of-products form is also called as Standard SOP.

SOP form representation is most suitable to use them in FPGA (Field Programmable Gate Arrays).


4.1.4: Experimental Analysis:

(i) Truth Table:

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0

1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

(ii) Circuit Diagram:

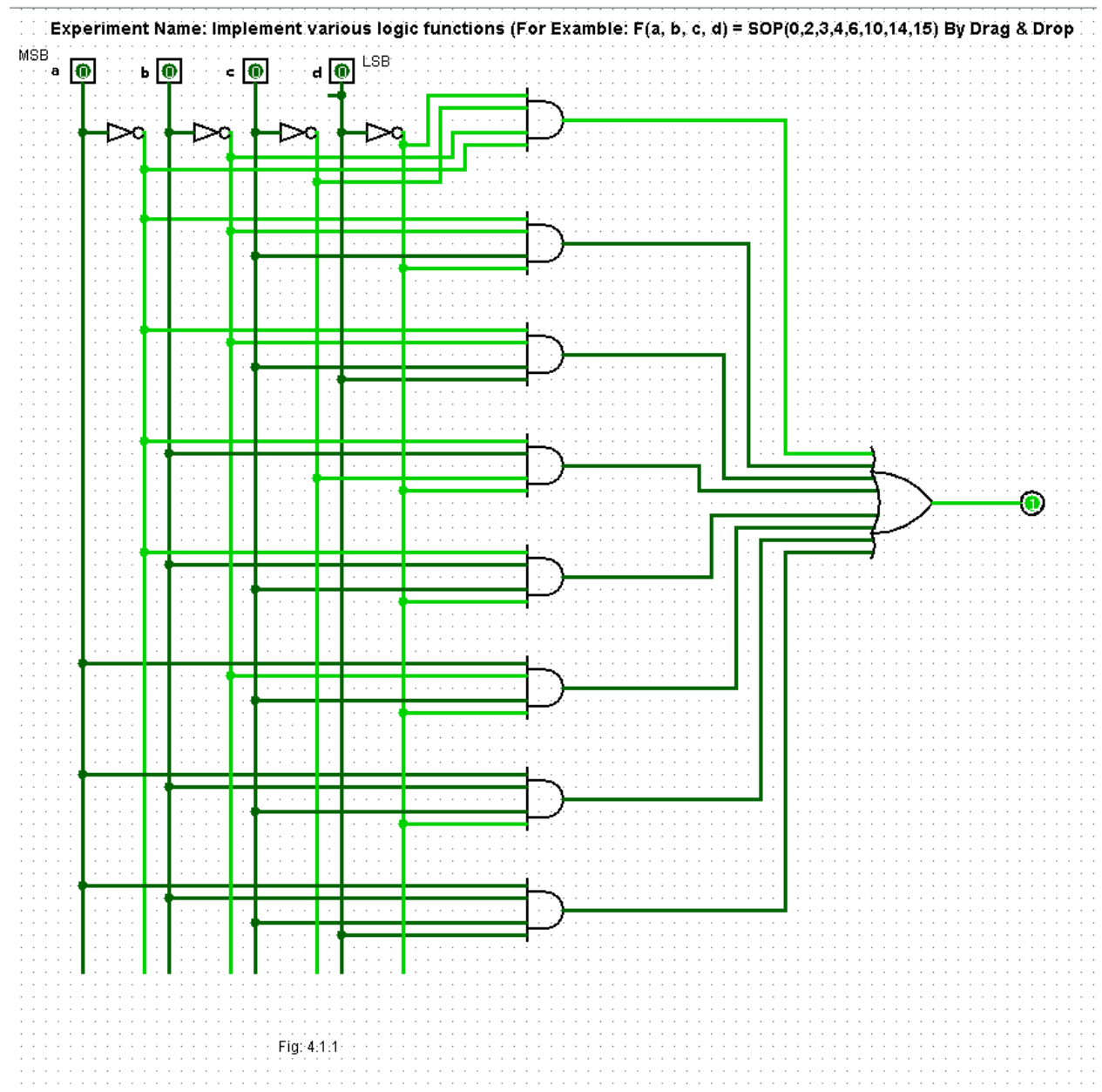

4.1.5: Conclusion:

The basic logic gates are the building blocks of more complex logic circuits. A Boolean function is an algebraic form of Boolean expression. In this experiment, a Boolean function in SOP form was implemented.

Thus the experiment was implemented successfully.

Experiment No.: 4.2

4.2.1: Name of the experiment:

Verify the result of simplified version of F in 1.

4.2.2: Objectives:

- To understand how to use the logisim software, test logic design and debug it.
- To study & implement various logic functions
- Simplifying logic circuit functions
- Understand how to implement simple circuits based on a schematic diagram using logic gates.

4.2.3: Theory:

A Boolean function is an algebraic form of Boolean expression. A Boolean function of n-variables is represented by $f(x_1, x_2, x_3, \dots, x_n)$. By using Boolean laws and theorems, we can simplify the Boolean functions of digital circuits. A brief note of different ways of representing a Boolean function is shown below.

- Sum-of-Products (SOP) Form
- Product-of-sums (POS) form
- Canonical forms

The logic function of F is simplified below:

$$\bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}\bar{d} + ab\bar{c}\bar{d} + abcd$$

$$= \bar{a}\bar{b}\bar{d}(c+\bar{c}) + \bar{a}\bar{b}cd + \bar{a}b\bar{d}(c+\bar{c}) + ac\bar{d}(b+\bar{b}) + abcd$$

$$= \bar{a}\bar{b}\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{d} + ac\bar{d} + abcd$$

$$= \bar{a}\bar{b}(\bar{d}+cd) + \bar{a}b\bar{d} + ac(\bar{d}+bd)$$

$$= \bar{a}\bar{b}(\bar{d}+c) + \bar{a}b\bar{d} + ac(\bar{d}+b)$$

$$= \bar{a}\bar{b}\bar{d} + \bar{a}\bar{b}c + \bar{a}b\bar{d} + ac\bar{d} + acb$$

$$= \bar{a}\bar{b}\bar{d} + \bar{a}b\bar{d} + \bar{a}\bar{b}c + ac\bar{d} + abc$$

$$= \bar{a}\bar{d}(\bar{b}+b) + \bar{a}\bar{b}c + ac\bar{d} + abc$$

$$= \bar{a}\bar{d} + \bar{a}\bar{b}c + ac\bar{d} + abc$$


$$= \bar{a}\bar{d} + ac\bar{d} + \bar{a}\bar{b}c + abc$$

4.2.4: Experimental Analysis:

(i) Truth Table:

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

(ii) Circuit Diagram:

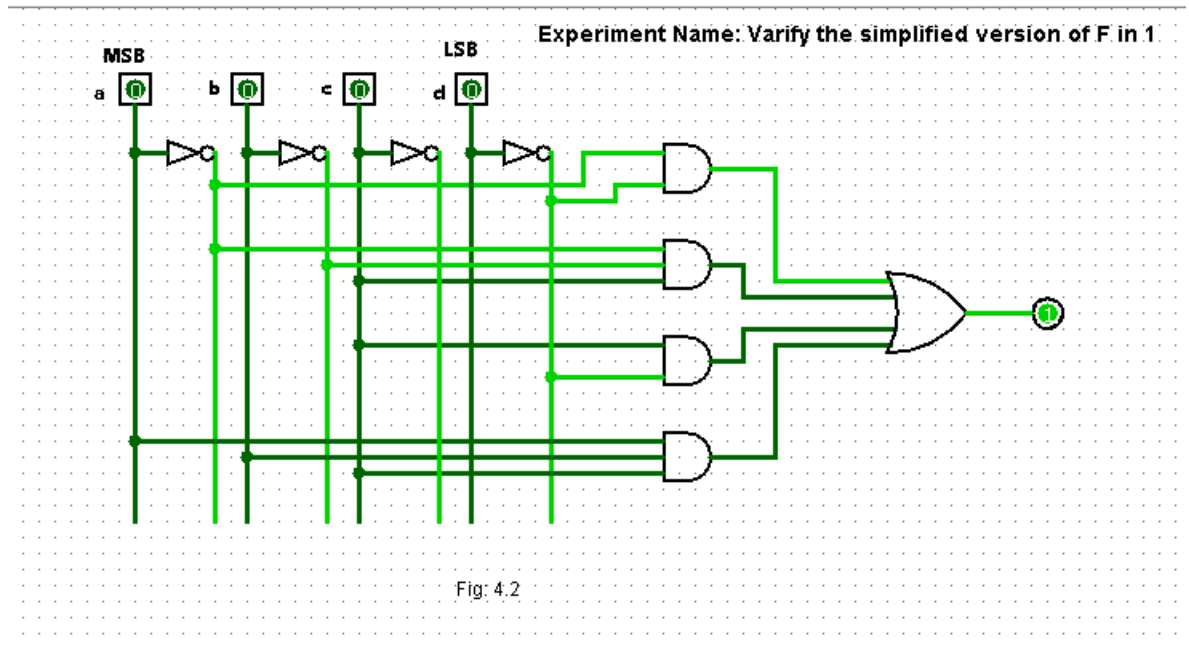

4.2.5: Conclusion:

The basic logic gates are the building blocks of more complex logic circuits. A Boolean function is an algebraic form of Boolean expression. A simplified Boolean function is needed to build a less complex circuit. So, the Boolean function is simplified here & implemented.

Thus the experiment was implemented successfully.